 


Brian Reber
CprE 381
Lab 02

Prelab:


5e)

```
entity loader is
  port (big_wank : in std_logic_vector(5 downto 0);
        net_tok  : in std_logic;
        tw_cnt   : in std_logic;
        clk      : in std_logic;
        assert   : out std_logic;
        data     : out std_logic_vector(9 downto 0);
        addr     : out std_logic_vector(7 downto 0);
        spud_out : out std_logic);
end loader;
```




6e)

 
7) In the entity declaration in part a, there is a missing semicolon at the end of the `clk` line, and there is also a missing semicolon at the end of the port declaration. In part b, there is a missing closing parenthesis and semicolon for the port declaration.



 Entity: ones_complimenter Architecture: structure Date: Wed Aug 31 02:45:52 PM CDT 2011 Row: 1 Page: 1



 Entity: ones_complimenter_df Architecture: dataflow Date: Wed Aug 31 02:46:11 PM CDT 2011 Row: 1 Page: 1




Entity:tb_ones_complimenter Architecture:behavior Date: Mon Sep 05 01:37:08 PM CDT 2011 Row: 1 Page: 1


These are a collection of waveforms for the one's complimenter. From looking at the waveforms, you can tell that it is behaving as expected (it is properly inverting bits).

Two-Input Mux

S	A	B	Out
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Expression: $S * A + \sim S * B$

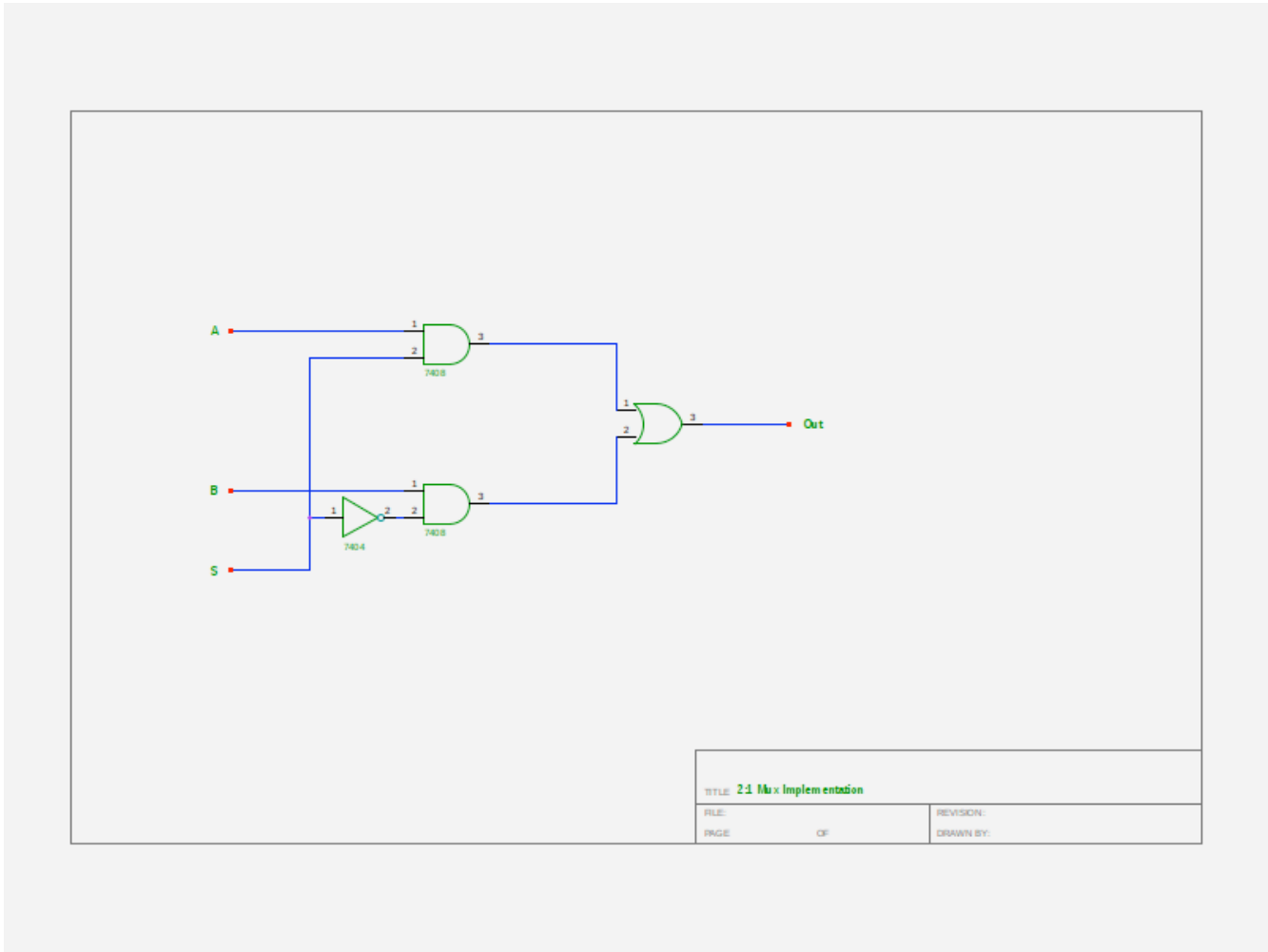


 


Full Adder


X	Y	Cin	Cout	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

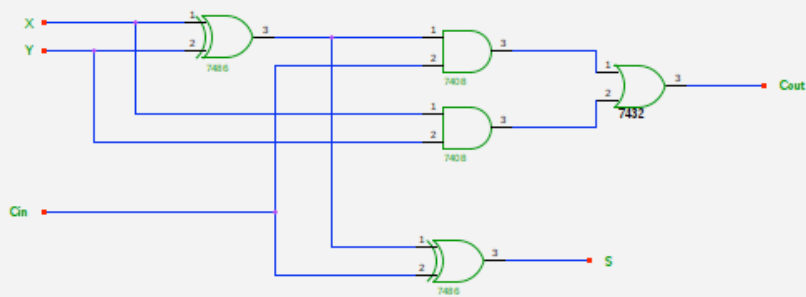Expression: $S = \sim X * \sim Y * C + \sim X * Y * \sim C + X * \sim Y * \sim C + X * Y * C = X \text{ xor } Y \text{ xor } C$
 $Cout = Y * C + X * C + X * Y = (Y \text{ xor } X) * C + X * Y$



 


Adder/Subtractor with Control

 

TITLE: AdderSubtractor with Control

FILE: PAGE OF REVISION: DRAWN BY:

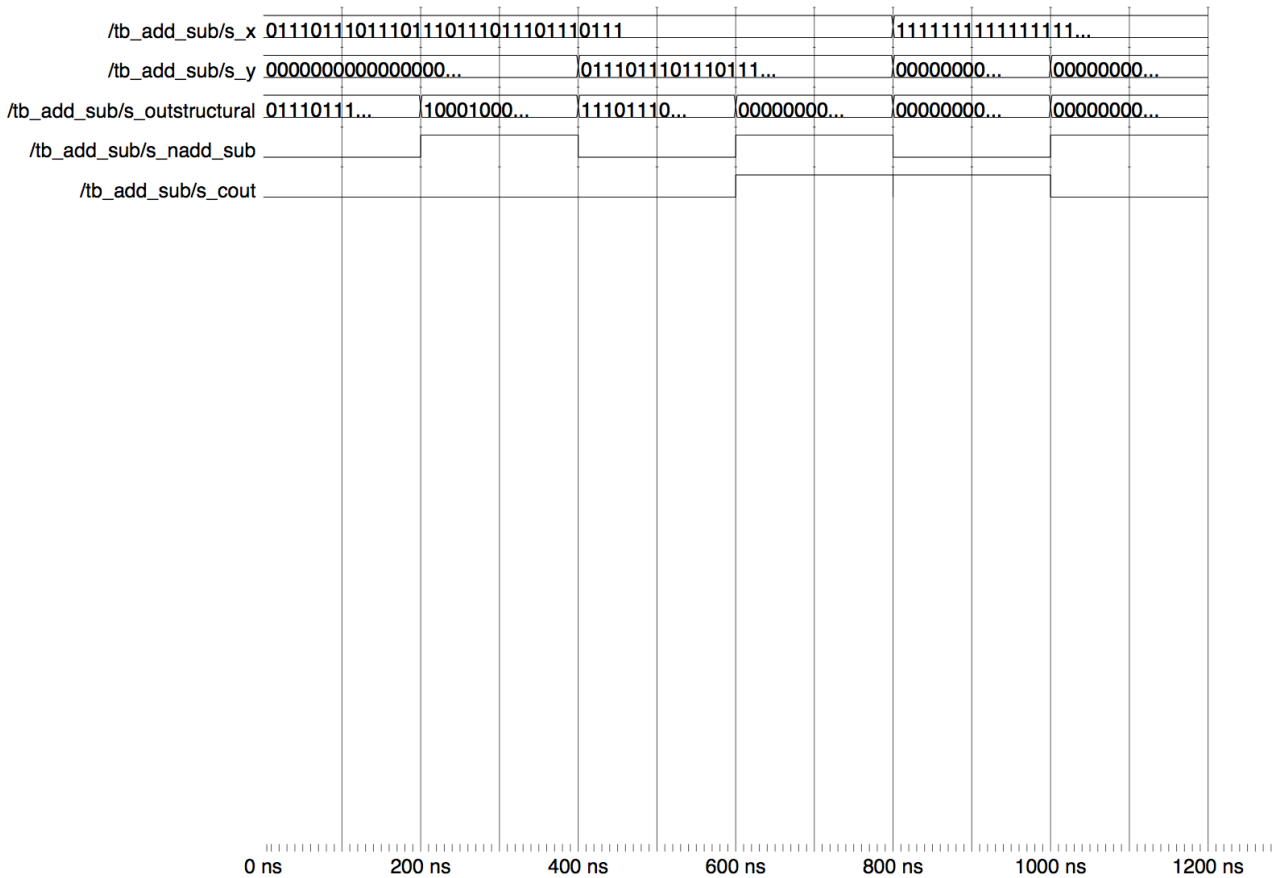This design uses an N-bit Adder, an N-bit 2:1 Mux and an N-bit inverter. If $nAdd_Sub = 0$, the mux will provide A to the adder, making it perform $A + B$. If $nAdd_Sub = 1$, the mux will give the adder the inverse of A (by using the N-bit inverter). It will also pass along 1 to the adder as the carry in bit, which causes it to perform the equivalent of $A - B$.



Entity:tb_add_sub Architecture:behavior Date: Mon Sep 05 06:11:09 PM CDT 2011 Row: 1 Page: 1

In this waveform, I have tested multiple values for the adder/subtractor unit. I tried to make test cases which would test different aspects of addition and subtraction including adding a positive and a negative number, subtracting a value from itself, adding two positive values, adding to make it overflow. See the `tb_add_sub.vhd` file for all of the values used, and their expected results.